



INDIAN INSTITUTE OF INFORMATION TECHNOLOGY,
DESIGN AND MANUFACTURING,
KANCHEEPURAM

RFMCD CIRCUIT DESIGN PRACTICE

MICROWAVE FILTER DESIGN

Nithesh

ESD19I008


Aim:

To design and analyze band pass and band reject filters.


Apparatus required:

ANSYS Electromagnetics Desktop

design:

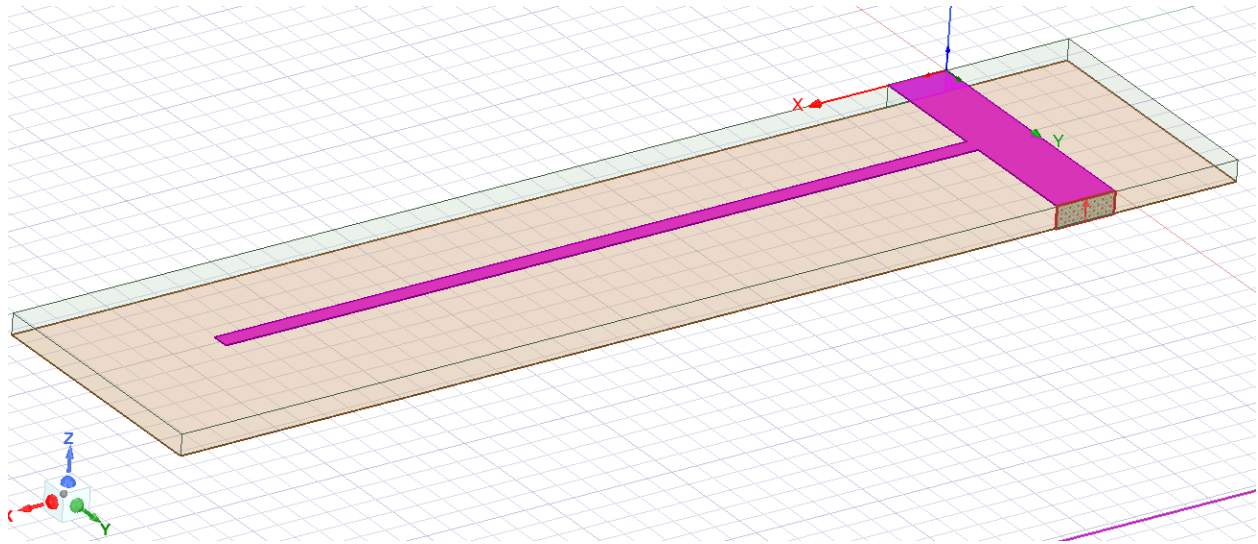


**Design a quarter wavelength resonator
stub-based band reject filter by
considering
stub impedance of 100 ohm
S parameter plot:**

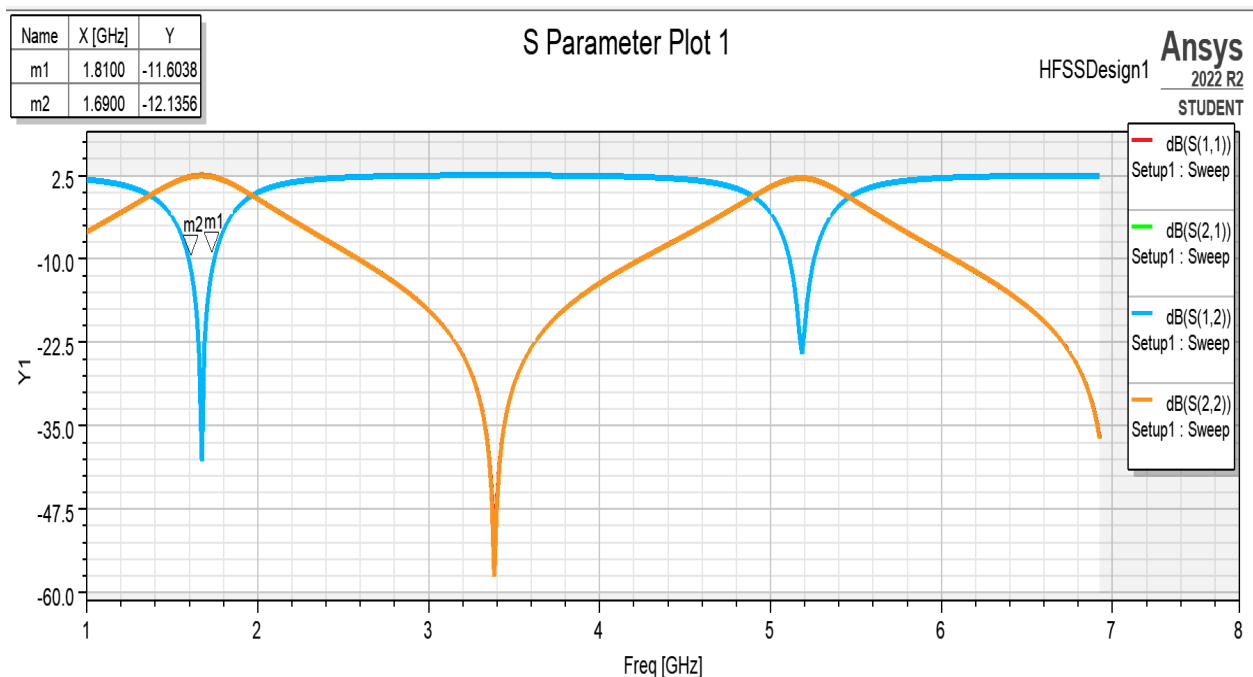


ACTIVITY 2:

Change stub element impedance to 50 ohm

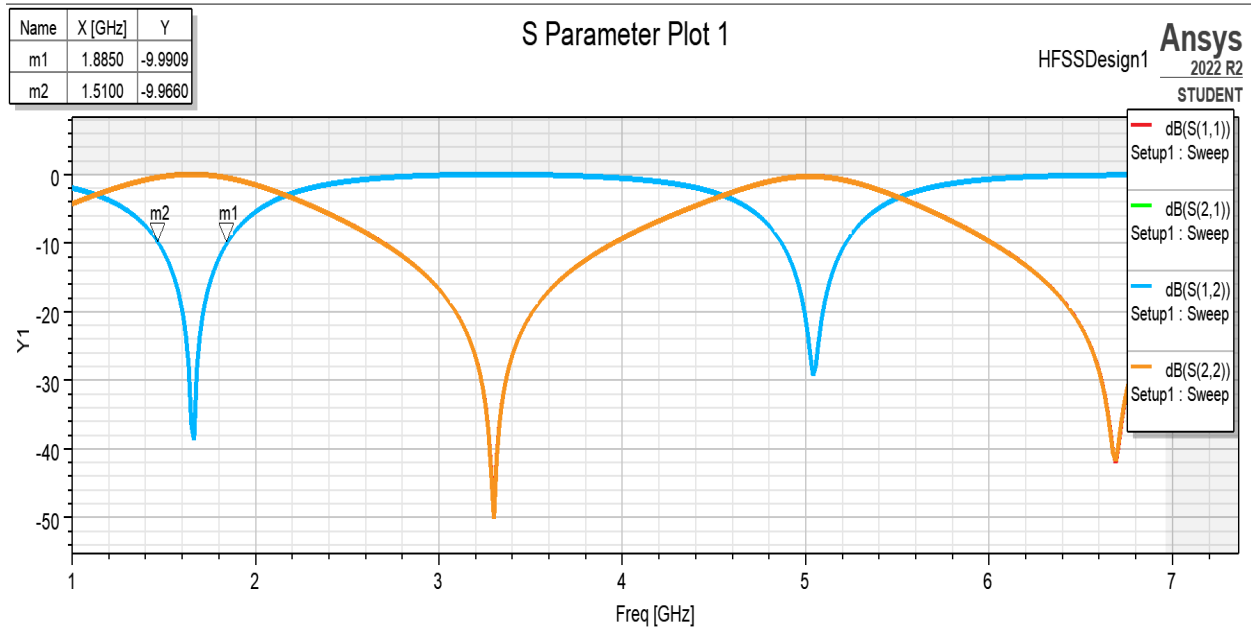


ACTIVITY 3:

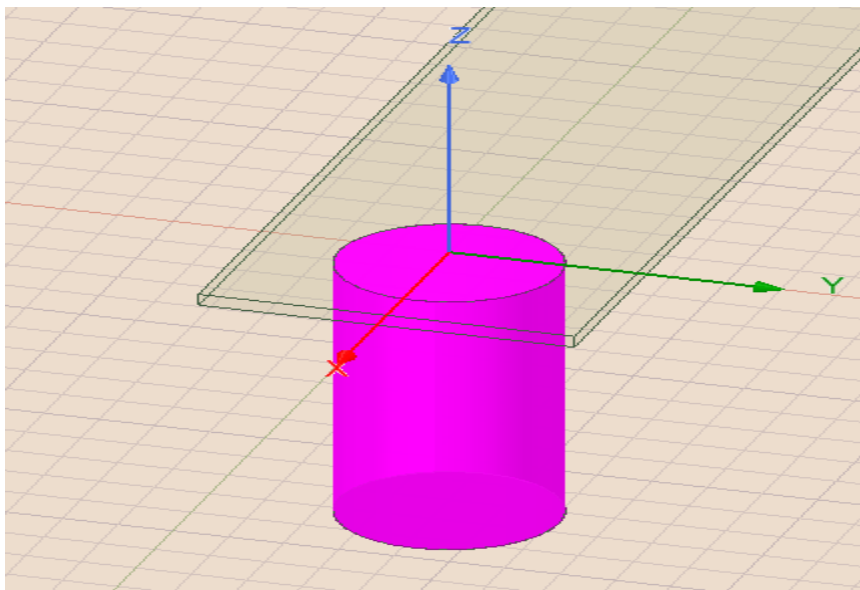Convert this filter to a band pass filter by putting a shorting post and analyze its response.




S parameter plot:

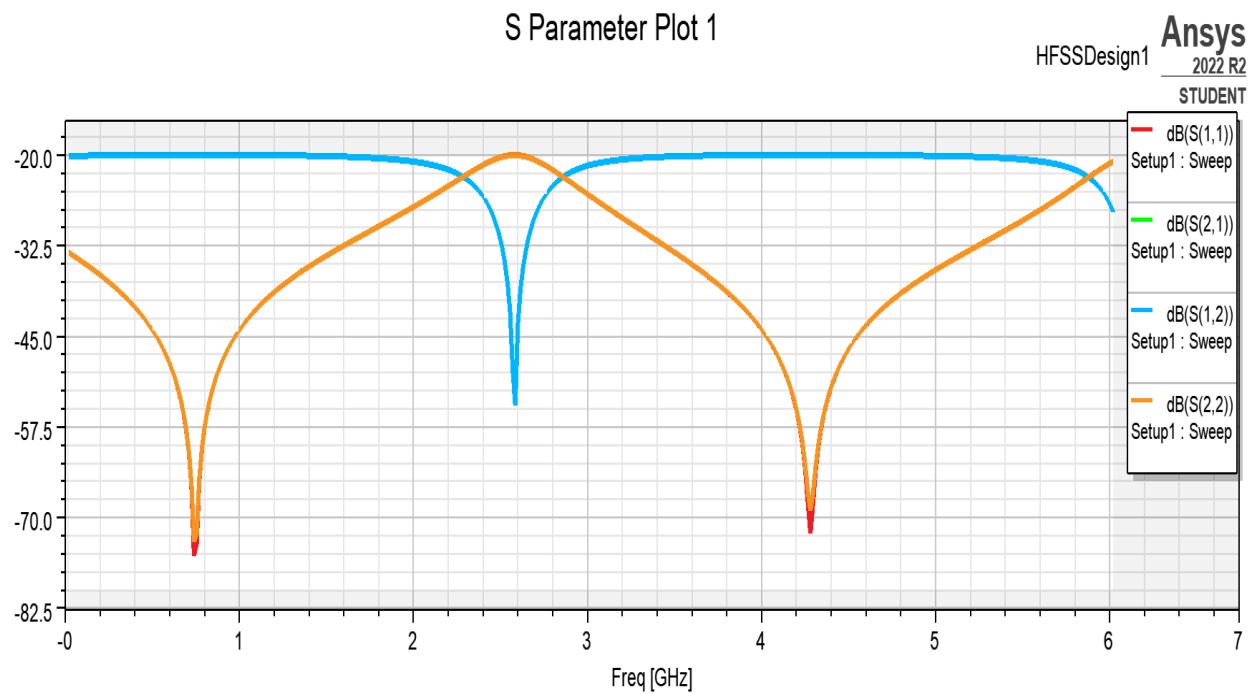


ACTIVITY 4:

LOW PASS FILTER:

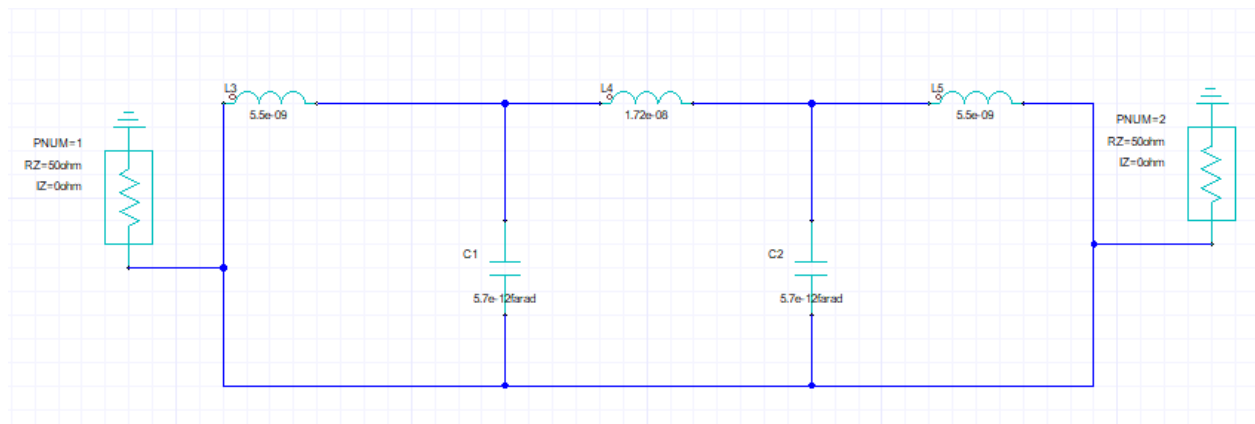

S parameter plot:

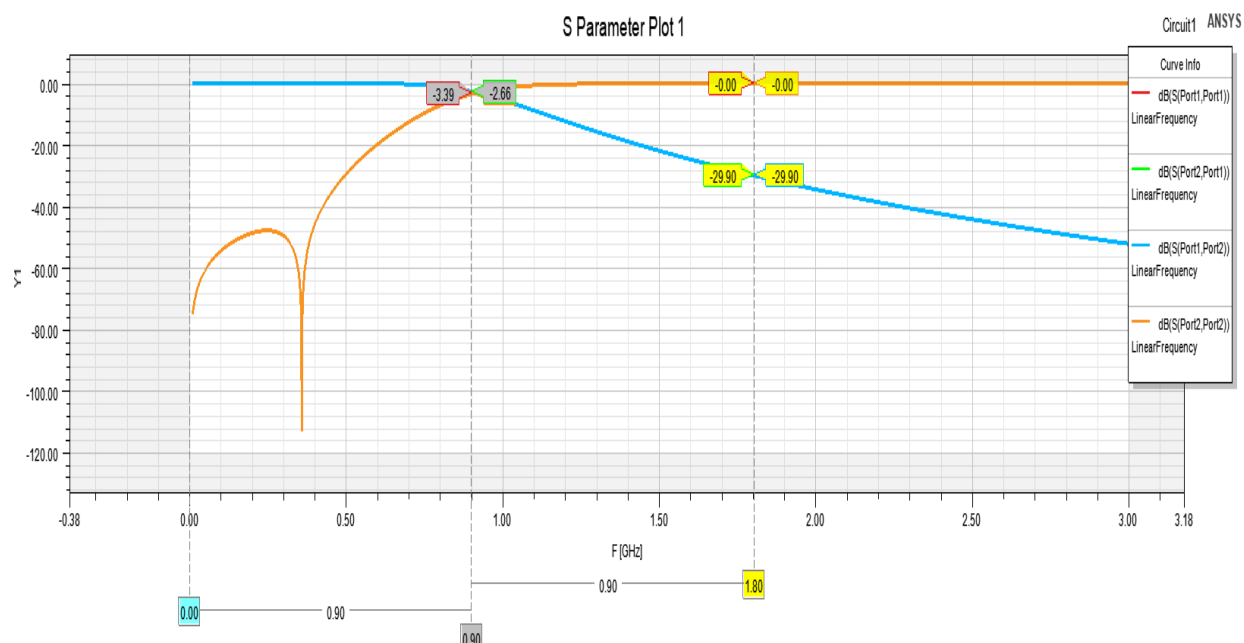

Inference:

- When stub impedance is matched to 100 or 50 ohms at 1.8GHz it acts as a band reject filter. For every odd multiples of 1.8GHz it acts as band reject filter rest of frequencies it acts as band pass filter.
- By putting a short it acts as a band pass filter. For every odd multiples of 1.8GHz it acts as band pass filter rest of frequencies it acts as band reject filter.
- At 1.8 GHz we can observe 30 db attenuation in activity 4.

Result:

Designed and analyzed band pass and band reject filters.